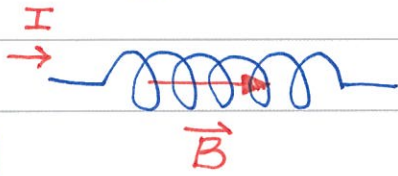




豪豬筆記

HH0126 Energy in Magnetic Field

An inductor is a circuit element that stores energy in the $\vec{B}$ field. Consider an ideal solenoid carrying current I .



The inductance is defined to be the proportionality constant that relates the current change $\frac{dI}{dt}$ to the EMF $\mathcal{E}$:

$$\mathcal{E} = -L \frac{dI}{dt}$$

According to Faraday's law, $\mathcal{E} = -\frac{d\Phi_B}{dt}$. Ignore the sign momentarily,

$$L \frac{dI}{dt} = \frac{d\Phi_B}{dt} \rightarrow LI = \Phi_B \rightarrow L = \frac{\Phi_B}{I}$$

We can now proceed to compute the inductance of the ideal solenoid $\odot$

$$B = \mu_0 NI / \ell \rightarrow \Phi_B = \underbrace{NBA}_{N \text{ coils!}} = (\mu_0 N^2 A / \ell) I$$


Define $n = N/\ell$ is the number of turns per unit length,

$$L = \frac{\Phi_B}{I} = \mu_0 A n^2 \ell$$

Like capacitance, the inductance only involves geometric factors —

the cross-sectional area A and the number of turns per unit length n . And, L is proportional to ℓ as expected $\odot$

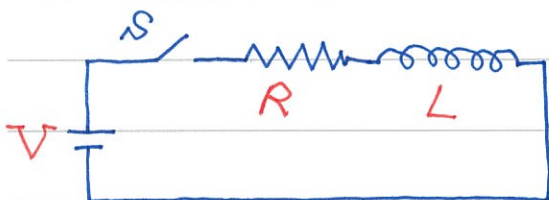① LR circuit Let us study a circuit with R and L in series as shown below. We close the switch S to



complete the circuit at $t=0$.

$$V - IR - L \frac{dI}{dt} = 0$$

$$\rightarrow L \frac{dI}{dt} = -R \left(I - \frac{V}{R} \right) \rightarrow \frac{dI}{dt} = -\left(\frac{R}{L} \right) \left(I - \frac{V}{R} \right)$$



豪豬筆記

page 2

Introduce the parameters: $I_\infty = V/R$ and $\tau_L = L/R$

$$\frac{dI}{dt} = -\frac{1}{\tau_L} (I - I_\infty) \rightarrow I - I_\infty = \text{const.} e^{-t/\tau_L}$$


Because the switch is turned on at $t=0$, we

expect that the initial current is zero, i.e. $I(0)=0$

The const above is thus $-I_\infty$ and the solution becomes

$$I(t) = I_\infty - I_\infty e^{-t/\tau_L} = I_\infty (1 - e^{-t/\tau_L})$$

what is the meaning of I_∞ ?

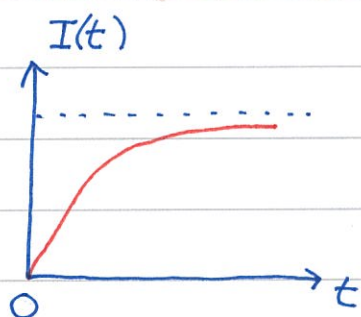

① Near $t=0$, $I \approx 0$. The voltage drop is mainly due to the inductor

$$\rightarrow V \approx L \frac{dI}{dt} \quad L \text{ dominates!}$$

② In the long-time limit, $t \rightarrow \infty$, $dI/dt \approx 0$ and the voltage drop is from the resistor R .

$$\rightarrow V \approx IR \quad R \text{ dominates}$$

Note that L is basically invisible for steady I

① Energy stored in $\vec{B}$ field. Let us multiply the differential equation of the LR circuit by current I . The LHS is

$$IV = I^2 R + L I \frac{dI}{dt}$$

just the power provided by the battery. The $I^2 R$ term

is the Ohmic dissipation power into thermal energy.

Thus, we expect the $L I dI/dt$ term must present the power into the inductor. Let U_B represent the energy stored in the magnetic field,

$$\frac{dU_B}{dt} = L I \frac{dI}{dt} \quad \text{or} \quad dU_B = L I dI$$

At $t=0$, there is

no current (and thus no magnetic field) in the circuit. It is natural to set $U_B=0$ when $I=0$.





豪豬筆記

The energy stored in the $\vec{B}$ field can be computed by integrating the differentials,

$$\int_0^{U_B} dU_B = L \int_0^I I dI \rightarrow U_B = \frac{1}{2} L I^2$$

Compare the above result with the energy stored in the $\vec{E}$ field of a capacitor, $U_E = \frac{1}{2C} Q^2$

One sees the similarity between

U_E and U_B clearly $\ddot{\circ}$ Because we can express U_E in terms of the electric field directly, we anticipate a similar expression should be available for the $\vec{B}$ field.


$$U_B = \frac{1}{2} L I^2 = \frac{1}{2} \mu_0 A \ell n^2 I^2 = \frac{1}{2\mu_0} (\mu_0 n I)^2 \cdot A \ell$$

Note that $\mu_0 n I = B$ is just the field inside the solenoid and $A \ell$ is the volume where $\vec{B} \neq 0$ $\ddot{\circ}$ Thus, the energy density in the $\vec{B}$ field u_B can be found,

$$u_B \equiv \frac{U_B}{V} = \frac{1}{2\mu_0} B^2 \quad \longleftrightarrow \quad u_E = \frac{1}{2} \epsilon_0 E^2$$

Again, the energy can be expressed in terms of the field without referring to the source $\ddot{\circ}$

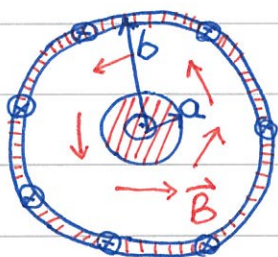Use a long coaxial cable as another demonstrating example. The currents in the central and the outer parts are the same but in opposite direction.



$$\oint \vec{B} \cdot d\vec{r} = \mu_0 I \rightarrow B = \frac{\mu_0 I}{2\pi r}$$

The energy density inside the cable is

$$u_B = \frac{1}{2\mu_0} B^2 = \frac{\mu_0 I^2}{8\pi^2 r^2}$$





豪豬筆記


page 4

The total energy U_B can be computed,

$$U_B = \int dV u_B = \int_a^b e \cdot 2\pi r dr \cdot \frac{\mu_0 I^2}{8\pi^2 r^2}$$

$$= \frac{\mu_0 I^2 e}{4\pi} \int_a^b \frac{dr}{r} \rightarrow \boxed{U_B = \frac{\mu_0 I^2 e}{4\pi} \ln \frac{b}{a}}$$

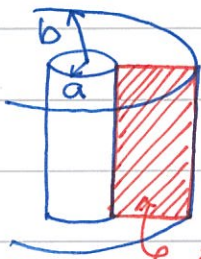On the other hand, one can try to compute U_B by inductance.



$$\Phi_B = \int B dA = \int_a^b \frac{\mu_0 I}{2\pi r} e \cdot dr = \frac{\mu_0 e I}{2\pi} \int_a^b \frac{dr}{r}$$

$$\rightarrow \Phi_B = \frac{\mu_0 e}{2\pi} \ln\left(\frac{b}{a}\right) \cdot I \rightarrow \boxed{L = \frac{\mu_0 e}{2\pi} \ln\left(\frac{b}{a}\right)}$$


Φ_B through this area $\odot$

Making use of the formula, $U_B = \frac{1}{2} L I^2$,

$$U_B = \frac{1}{2} \cdot \frac{\mu_0 e}{2\pi} \ln\left(\frac{b}{a}\right) I^2 = \frac{\mu_0 e I^2}{4\pi} \ln \frac{b}{a} \leftarrow \text{the same result } \odot$$

Even though we just work out two examples (solenoid and coaxial cable), the expression of the energy stored in the $\vec{B}$ field, $u_B = (\frac{1}{2}\mu_0) B^2$ is true in general.

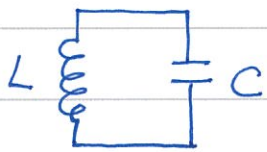① Electromagnetic oscillation. Consider a LC circuit without any dissipation. The voltage across the capacitor equals the EMF of the inductor,



$$\boxed{\frac{Q}{C} + L \frac{dI}{dt} = 0} \rightarrow \frac{Q}{C} + L \frac{d^2 Q}{dt^2} = 0$$

Introduce the EM oscillation frequency of the circuit,

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$\rightarrow \frac{d^2 Q}{dt^2} + \omega_0^2 Q = 0 \quad \text{just like the SHO } \odot$$

The solution of the above differential equation is

$$\boxed{Q(t) = Q_M \cos(\omega_0 t + \phi)}$$

Q_M is the maximum charge in the capacitor.





豪豬筆記


page 5

By differentiation, the oscillating current is

$$I(t) = \frac{dQ}{dt} = -\omega_0 Q_M \sin(\omega_0 t + \phi)$$

We are ready to compute U_E and U_B in the LC circuit now :
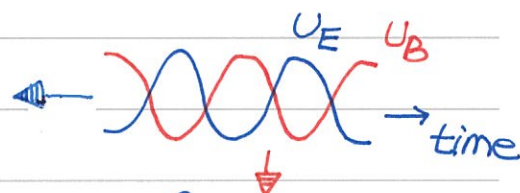
$$U_E = \frac{1}{2C} Q^2 = \frac{Q_M^2}{2C} \cos^2(\omega_0 t + \phi)$$



$$U_B = \frac{1}{2} L I^2 = \frac{1}{2} L \omega_0^2 Q_M^2 \sin^2(\omega_0 t + \phi) = \frac{Q_M^2}{2C} \sin^2(\omega_0 t + \phi)$$

It is easy to see that the total energy is constant,

$$U = U_E + U_B = \frac{Q_M^2}{2C} [\cos^2(\omega_0 t + \phi) + \sin^2(\omega_0 t + \phi)] = \frac{Q_M^2}{2C}$$

The energies in the electric and the magnetic field transform into each other and lead to the electromagnetic oscillation.



清大東院

2014.04/0

