

Boolean Algebra and Logic Gates

Hsi-Pin Ma 馬席彬

<https://eeclass.nthu.edu.tw/course/3452>

Department of Electrical Engineering
National Tsing Hua University

Outline

- Algebraic Properties
- Boolean Algebra
- Two-valued Boolean Algebra
- Basic Theorems and Properties of Boolean Algebra
- Boolean Functions
- Normal and Standard Forms
- Other Logic Operations

Algebraic Properties

Basic Definition

- A *set* is a collection of objects with a common property.
- A *binary operator* on a set S is a rule that assigns to, each pair of elements in S , another unique element in S .
- The *axioms (postulates)* of an algebra are the basic assumptions from which all theorems of the algebra can be proved.
- It is assumed that there is an *equivalent relation* ($=$), which satisfies that *principle of substitution*.
 - It is *reflexive, symmetric, and transitive*.

Most Common Axioms Used to Formulate an Algebra Structure (1/2)

- Closure

- A set S is closed with respect to a binary operator $*$ if and only if $\forall x, y \in S, (x * y) \in S$

- Associativity

- A binary operator $*$ on S is associative if and only if $\forall x, y, z \in S, (x * y) * z = x * (y * z)$

- Commutativity

- A binary operator $*$ defined on S is commutative if and only if $\forall x, y \in S, x * y = y * x$

Most Common Axioms Used to Formulate an Algebra Structure (2/2)

- Identity element

- A set S has an identity element with respect to $*$ if and only if $\exists e \in S$ such that $\forall x \in S, e * x = x * e = x$

- Inverse element

- A set S having the identity element e with respect to $*$ has an inverse if and only if $\forall x \in S, \exists y \in S$ such that $x * y = e$

- Distributivity

- If $*$ and \bullet are binary operators on S , $*$ is distributive over \bullet if and only if $\forall x, y, z \in S, x * (y \bullet z) = (x * y) \bullet (x * z)$

Example: A Field

- A field is a set of elements, together with two binary operators.
- The set of real numbers together with the binary operators $+$ and \bullet , forms the field of real numbers.
 - ‘ $+$ ’ defines addition.
 - The additive identity is 0.
 - The additive inverse defines the subtraction.
 - The binary operator \bullet defines multiplication.
 - The multiplicative identity is 1.
 - For $a \neq 0$, $1/a$ (the multiplicative inverse of a) defines division.
 - The only distributive law applicable is that of \bullet over $+$

$$a \cdot (b + c) = a \cdot b + a \cdot c$$

Boolean Algebra

Axiomatic Definition

- Boolean algebra

- An algebraic system of logic introduced by George Boole in 1854

- Switching algebra

- A 2-valued Boolean algebra introduced by Claude Shannon in 1938

- ★• Huntington postulates

- A formal definition of Boolean Algebra in 1904
 - Defined on a set B with binary operators $+$ and \bullet , and the equivalence relation $=$.

Huntington Postulates (1/2)

- Defined by a set B with binary operators $+$ and \cdot
 - Closure with respect to $+$ and \cdot • (P1)
 - $x, y \in B \Rightarrow x + y \in B, x \cdot y \in B$
 - An identity element with respect to $+$ and \cdot • (P2)
 - $0 + x = x + 0 = x, 1 \cdot x = x \cdot 1 = x$
 - Commutative with respect to $+$ and \cdot • (P3)
 - $x + y = y + x, x \cdot y = y \cdot x$

Huntington Postulates (2/2)

- Distributive over $+$ and \bullet **(P4)**
 - $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$
 - $x + (y \cdot z) = (x + y) \cdot (x + z)$
- $\forall x \in B, \exists x' \in B$ (called the *complement* of x) such that $x + x' = 1, x \cdot x' = 0$ **(P5)**
- There are *at least* 2 distinct elements in B **(P6)**
 - *There exist at least two $x, y \in B$, such that $x \neq y$*

Notes (1 / 2)

- The axioms are *independent*, none can be proved from others.
- *Associativity* is not included, since it can be derived (both $+$ and \bullet) from the given axioms.
- In *ordinary algebra*, $+$ is *not distributive* over \bullet .
- No *additive* or *multiplicative* inverses; no subtraction or division operations.
- Complement is *not available* in ordinary algebra.
- B is as yet undefined. It is to be defined as the set $\{0,1\}$ (*two-valued Boolean Algebra*). In ordinary algebra, the set S can contain an infinite set of elements.

Notes (2/2)

- Boolean algebra

- Set B of at least 2 elements (not *variables*)
- Rules of operation for the 2 binary operators (+ and \bullet)
- Huntington postulates satisfied by the elements of B and the operators.

- Two-valued Boolean algebra (switching algebra)

- $B \equiv \{0, 1\}$
- The binary operators are defined as the logical AND (\bullet) and OR (+). For convenience, a unary operation NOT (complement) is also included for basic operations.
- The Huntington postulates are still valid.

- Unless otherwise noted, we will use the term *Boolean algebra* for the *2-valued Boolean algebra*.

Two-valued Boolean Algebra

Two-valued Boolean Algebra

- $B \equiv \{0, 1\}$ is the set.
- The binary operator for + and \cdot , and the unary operator *complement*.

input		output
x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

input		output
x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

input	output
x	x'
0	1
1	0

Huntington Postulates Test (1/3)

- Closure

- $\{0,1\}$ of the operator results still in B .

- Identity elements

- $0 + 0 = 0, 0 + 1 = 1 + 0 = 1$ (0: identity of +)

- $1 \cdot 1 = 1, 1 \cdot 0 = 0 \cdot 1 = 0$ (1: identity of \bullet)

- Commutative

- Obviously from the table

Huntington Postulates Test (2/3)

• Distributive

– Holds for \bullet over $+$

x	y	z	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

– Can be shown to hold for $+$ over \bullet .

Huntington Postulates Test (3/3)

- Complement

- $x + x' = 1$ since $0 + 0' = 0 + 1 = 1$ and $1 + 1' = 1 + 0 = 1$

- $x \cdot x' = 0$ since $0 \cdot 0' = 0 \cdot 1 = 0$ and $1 \cdot 1' = 1 \cdot 0 = 0$

- The two-valued Boolean algebra has two distinct elements, 0 and 1, with $0 \neq 1$.



Basic Theorems and Properties of Boolean Algebra

Duality

- Every algebraic expression deducible from the postulates of Boolean algebra remains valid if the *operators* and *identity elements* are *interchanged*.
 - Binary operators: AND \Leftrightarrow OR
 - Identity elements: 1 \Leftrightarrow 0

Postulates and Theorems of Boolean Algebra

(a)

(b)

P2	$x+0 = x$	$x \cdot 1 = x$
p5	$x+x' = 1$	$x \cdot x' = 0$
T1	$x + x = x$	$x \cdot x = x$
T2	$x + 1 = 1$	$x \cdot 0 = 0$
T3, involution	$(x')' = x$	
p3, commutative	$x+y = y+x$	$x \cdot y = y \cdot x$
T4, associative	$x+(y+z)=(x+y)+z$	$x \cdot (y \cdot z)=(x \cdot y) \cdot z$
P4, distributive	$x \cdot (y+z)=x \cdot y+x \cdot z$	$x+y \cdot z=(x+y) \cdot (x+z)$
T5, DeMorgan	$(x+y)' = x' \cdot y'$	$(x \cdot y)' = x'+y'$
T6, absorption	$x+x \cdot y = x$	$x \cdot (x+y) = x$

Basic Theorems (1/5)

• Theorem 1 (Idempotency)

– (a) $x + x = x$, (b) $x \cdot x = x$

	<i>Statement</i>	<i>Justification</i>
$x + x$	$= (x + x) \cdot 1$	postulate 2(b)
	$= (x + x)(x + x')$	5(a)
	$= x + xx'$	4(b)
	$= x + 0$	5(b)
	$= x$	2(a)

	<i>Statement</i>	<i>Justification</i>
$x \cdot x$	$= xx + 0$	postulate 2(a)
	$= xx + xx'$	5(b)
	$= x(x + x')$	4(a)
	$= x \cdot 1$	5(a)
	$= x$	2(b)

Basic Theorems (2/5)

• Theorem 2

$$(a) x + 1 = 1, \quad (b) x \cdot 0 = 0$$

Statement

Justification

$x + 1$	$= 1 \cdot (x + 1)$	postulate 2(b)
	$= (x + x')(x + 1)$	5(a)
	$= x + x' \cdot 1$	4(b)
	$= x + x'$	2(b)
	$= 1$	5(a)

– (b) can be proved by duality

Basic Theorems (3/5)

- Theorem 3 (Involution)

$$(x')' = x$$

- P5 defines the complement of x , and the complement of x' is both x and $(x')'$

- Theorem 4 (Associativity)

$$\text{(a)} \quad x + (y + z) = (x + y) + z, \quad \text{(b)} \quad x(yz) = (xy)z$$

- Can be proved by truth table

Basic Theorems (4/5)

- Theorem 5 (DeMorgan's Theorem)

- (a) $(x + y)' = x' \cdot y'$, (b) $(xy)' = x' + y'$

- Duality principle

x	y	x+y	$(x+y)'$	x'	y'	$x'y'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

Basic Theorems (5/5)

• Theorem 6 (Absorption)

– (a) $x + xy = x$, (b) $x(x + y) = x$

	<i>Statement</i>	<i>Justification</i>
$x + xy$	$= x \cdot 1 + xy$	postulate 2(b)
	$= x(1 + y)$	4(a)
	$= x(y + 1)$	3(a)
	$= x \cdot 1$	2(a)
	$= x$	2(b)

Operator Priority

- Operator precedence

- Parentheses

- NOT

- AND

- OR

- Examples

- $xy' + z$

- $(xy + z)'$

Boolean Functions

Boolean Functions

- A Boolean function is an algebraic expression formed with

- Binary variables
- Logic operators AND, OR
- Unary NOT
- Parentheses
- An equal sign

- Examples

- $F_1 = x + y'z$

- $F_2 = x'y'z + x'yz + xy'$

x	y	z	F ₁	F ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0



Boolean Functions

- Can be represented by a truth table, with 2^n rows in the table (n: # of variable in the function)
- There are infinitely many algebraic expressions that specify a given Boolean function. It's important to find the *simplest* one. (cost)
- Any Boolean function can be transformed in a straightforward manner from an algebraic expression into a *logic diagram* of only AND, OR, and NOT gates.


Gate Implementation

- Logic diagrams

$$F_1 = x + y'z$$

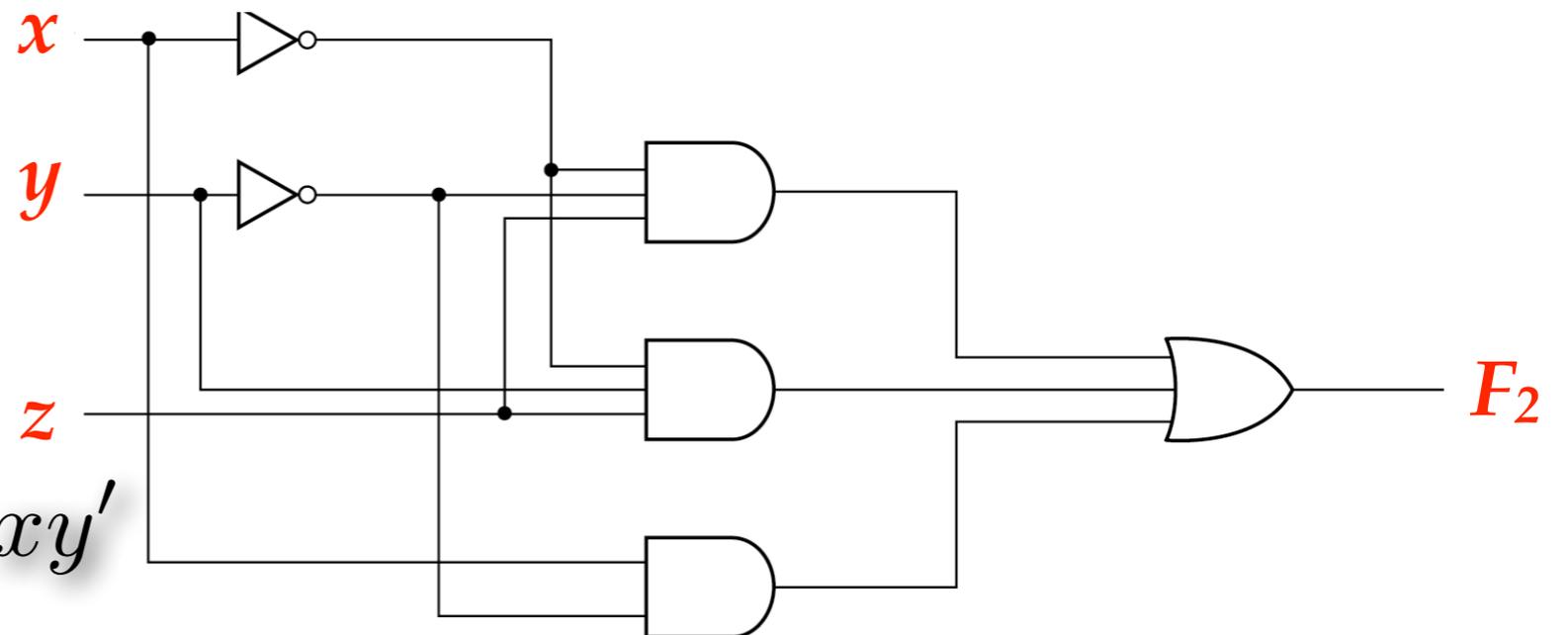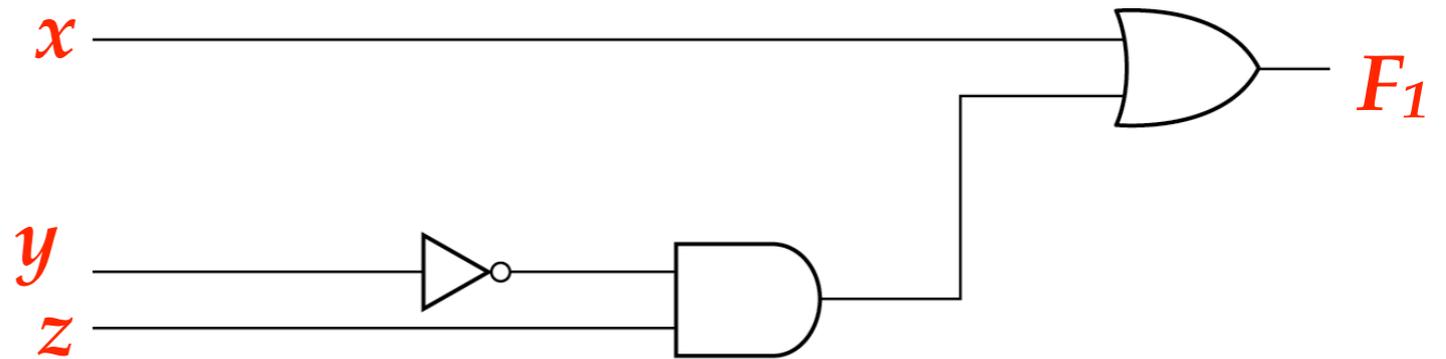

$$F_2 = x'y'z + x'yz + xy'$$

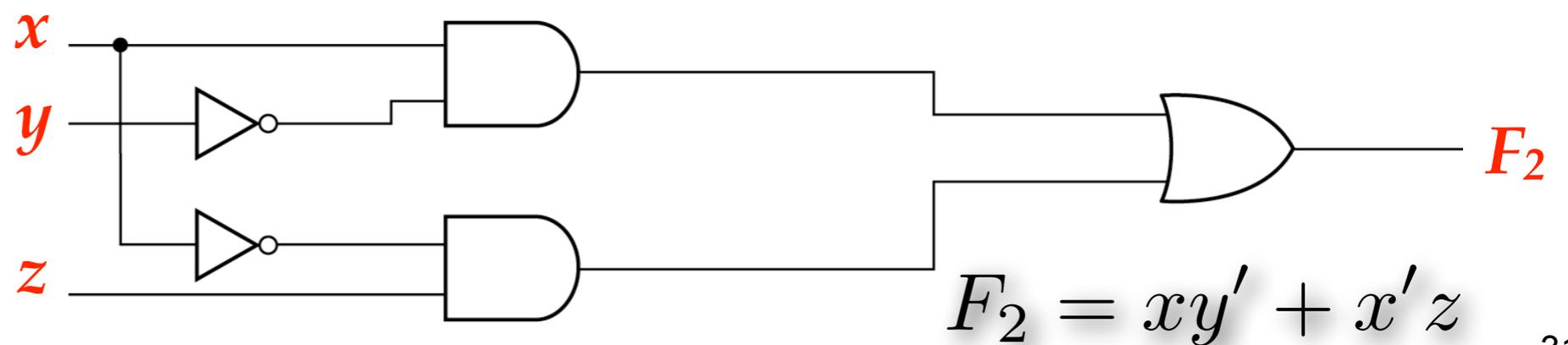

$$F_2 = xy' + x'z$$

Boolean Functions

- A *literal* is a *variable* or its complement in a Boolean expression
 - $F_2 = x'y'z + x'yz + xy'$
 - 8 literals,
 - 1 OR term (sum term) and 3 AND terms (product terms).
 - literal: a input to a gate, term: implementation with a gate
- The complement of any function F is F' , which can be obtained by DeMorgan's Theorem.
 - Take the dual of F , and then complement each literal in F .
 - $F_2' = (x'y'z + x'yz + xy')' = (x + y + z')(x + y' + z')(x' + y)$

Algebraic Manipulation (1 / 2)

- Minimize the number of literals and terms for a simpler circuits (less expensive)
- Algebraic manipulation can minimize literals and terms. However, no specific rules to guarantee the optimal results.
- CAD tools for logic minimization are commonly used today.

Algebraic Manipulation (2/2)

- Some useful rules

- $x(x' + y) = xy$

- $x + x'y = x + y$

- $xy + yz + x'z = xy + x'z$ (the Consensus Theorem I)

- $(x + y)(y + z)(x' + z) = (x + y)(x' + z)$ (the Consensus Theorem II, duality from Consensus Theorem I)

Canonical and Standard Forms

Minterms and Maxterms

- Minterm (m_i) (or *standard product term*)
 - An AND (product) term consists of all literals (each appears exactly **once**) in their normal form or in their complement form, but not in both
 - eg. two binary variable x and y , the minterms are xy , xy' , $x'y$, $x'y'$
 - n variable can be combined to form 2^n minterms
- Maxterms (M_i) (or *standard sum term*)
 - An OR (sum) term consists of all literals (each appears exactly **once**) in their normal form or in their complement form, but not in both
 - eg. two binary variable x and y , the maxterms are $x+y$, $x+y'$, $x'+y$, $x'+y'$
- Each maxterm is the complement of its corresponding minterm and vice versa. ($M_i = m_i'$)

Minterms and Maxterms

• Canonical forms

- sum-of-minterms (som)
- product-of-maxterms (pom)

	x y z	Minterms	Notation	Maxterms	Notation
0	0 0 0	$x'y'z'$	m_0	$x+y+z$	M_0
1	0 0 1	$x'y'z$	m_1	$x+y+z'$	M_1
2	0 1 0	$x'yz'$	m_2	$x+y'+z$	M_2
3	0 1 1	$x'yz$	m_3	$x+y'+z'$	M_3
4	1 0 0	$xy'z'$	m_4	$x'+y+z$	M_4
5	1 0 1	$xy'z$	m_5	$x'+y+z'$	M_5
6	1 1 0	xyz'	m_6	$x'+y'+z$	M_6
7	1 1 1	xyz	m_7	$x'+y'+z'$	M_7

Example

x	y	z	f ₁	f ₂	f ₁ '	f ₂ '
0	0	0	0	0	1	1
0	0	1	1	0	0	1
0	1	0	0	0	1	1
0	1	1	0	1	1	0
1	0	0	1	0	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	0	0

- A Boolean function can be expressed by

- a truth table

- sum-of-minterms

- $f_1 = x'y'z + xy'z' + xyz$
 $= m_1 + m_4 + m_7 = \sum (1, 4, 7)$

- $f_2 = x'yz + xy'z + xyz' + xyz$
 $= m_3 + m_5 + m_6 + m_7 = \sum (3, 5, 6, 7)$

- product-of-maxterms

- $f_1 = (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z')(x' + y' + z)$
 $= M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = \Pi(0, 2, 3, 5, 6)$

- $f_2 = (x + y + z)(x + y + z')(x + y' + z)(x' + y + z)$
 $= M_0 \cdot M_1 \cdot M_2 \cdot M_4 = \Pi(0, 1, 2, 4)$

Canonical Forms

- Any function can be represented by either of the 2 canonical forms
 - To convert from one canonical form to another, interchange Σ and Π , and list the numbers that were excluded from the original form.
 - $f_1 = \Sigma (1, 4, 7)$ is the sum of 1-minterms for f_1 .
 - $f_1' = \Sigma (0, 2, 3, 5, 6)$ is the sum of 0-minterms for f_1 .
- How to convert $f=x+yz$ into canonical form?
 - by truth table
 - by expanding the missing variables in each term, using $1=x+x'$, $0=xx'$

Standard Forms

- Canonical forms are seldom used.
- Standard forms
 - sum-of-products (sop)
 - Product terms (implicants) are the AND terms, which can have fewer literals than the minterms.
 - product-of-sums (pos)
 - Sum terms are the OR terms, which can have fewer literals than maxterms.
- Standard forms are not unique!

Standard Forms

- Standard form examples

- $f_1 = xy + xy'z + x'yz$ (sop form)

- $f_1' = (x' + y')(x' + y + z')(x + y' + z')$ (pos form)

- Nonstandard forms can have fewer literals than standard forms

- $xy + xy'z + xy'w = x(y + y'z + y'w) = x(y + y'(z + w))$

- $xy + yz + zx = xy + (x + y)z = x(y + z) + yz = xz + y(x + z)$

Other Gate Types

Other Logic Operations

- For n binary variables
 - 2^n rows in the truth table
 - 2^{2^n} functions
 - 16 different Boolean functions if $n=2$
- All the new symbols except for the XOR are not in common use by digital designers

Truth Tables for the 16 Functions of Two Binary Variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Boolean Expressions for the 16 Functions of Two Variables







Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x , but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y , but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y , but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \subset y$	Implication	If y , then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x , then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

Digital Logic Gates







- Consider 16 functions

- Two functions generate constants
 - Null / Zero, Identity / One
- Four one-variable functions
 - Complement (inverter) , Transfer (buffer)
- 10 functions that define 8 specific binary functions
 - AND, Inhibition, XOR, OR, NOR, Equivalence (XOR), Implication, NAND
 - Inhibition and Implication are neither commutative nor associative
 - NAND and NOR are commutative but not associative

Primitive Digital Logic Gates


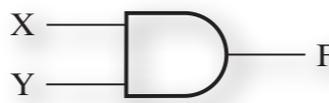
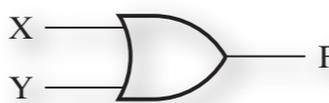
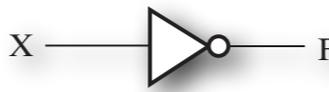
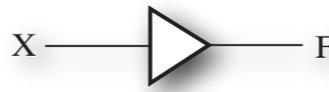
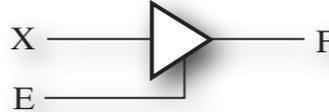
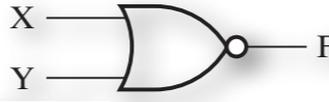
Name	Distinctive-Shape Graphics Symbol	Algebraic Equation	Truth Table															
AND		$F = XY$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	X	Y	F	0	0	0	0	1	0	1	0	0	1	1	1
X	Y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = X + Y$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	1
X	Y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT (inverter)		$F = \bar{X}$	<table border="1"> <thead> <tr> <th>X</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	X	F	0	1	1	0									
X	F																	
0	1																	
1	0																	
Buffer		$F = X$	<table border="1"> <thead> <tr> <th>X</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	X	F	0	0	1	1									
X	F																	
0	0																	
1	1																	
3-State Buffer			<table border="1"> <thead> <tr> <th>E</th> <th>X</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>Hi-Z</td></tr> <tr><td>0</td><td>1</td><td>Hi-Z</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	E	X	F	0	0	Hi-Z	0	1	Hi-Z	1	0	0	1	1	1
E	X	F																
0	0	Hi-Z																
0	1	Hi-Z																
1	0	0																
1	1	1																
NAND		$F = \overline{X \cdot Y}$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	X	Y	F	0	0	1	0	1	1	1	0	1	1	1	0
X	Y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = \overline{X + Y}$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

Complex Digital Logic Gates

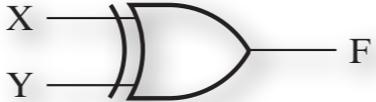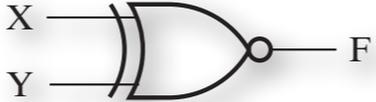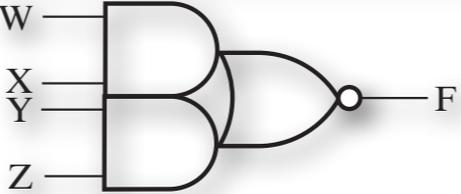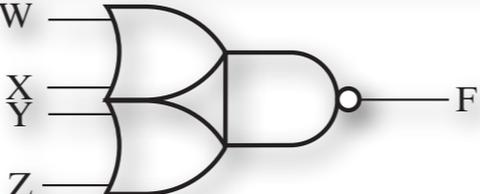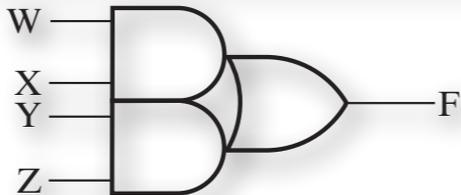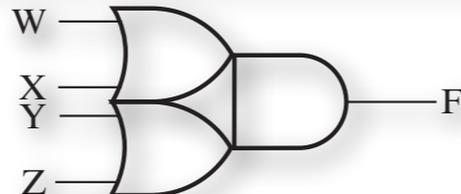Name	Distinctive-Shape Graphics Symbol	Algebraic Equation	Truth Table															
Exclusive-OR (XOR)		$F = X\bar{Y} + \bar{X}Y$ $= X \oplus Y$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	0
X	Y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR (XNOR)		$F = \overline{X\bar{Y} + \bar{X}Y}$ $= X \oplus Y$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	1
X	Y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																
AND-OR-INVERT (AOI)		$F = \overline{WX + YZ}$																
OR-AND -INVERT (OAI)		$F = \overline{(W + X)(Y + Z)}$																
AND-OR (AO)		$F = WX + YZ$																
OR-AND (OA)		$F = (W + X)(Y + Z)$																

Eight Basic Digital Logic Gates

typical CMOS implementation

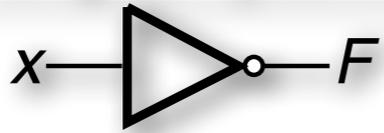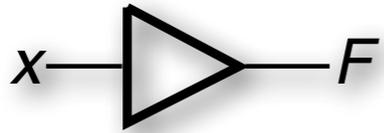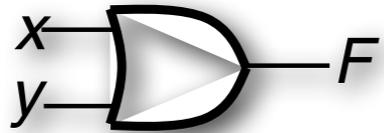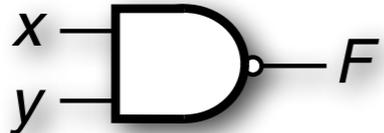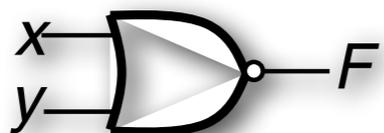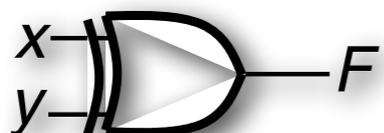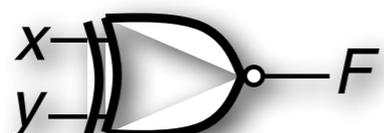Name	Graphic symbol	Function	No. transistors	Gate delay (ns)
			cost	performance
Inverter		$F = x'$	2	1
Driver		$F = x$	4	2
AND		$F = xy$	6	2.4
OR		$F = x + y$	6	2.4
NAND		$F = (xy)'$	4	1.4
NOR		$F = (x + y)'$	4	1.4
XOR		$F = x \oplus y$	14	4.2
XNOR		$F = x \odot y$	12	3.2


[Gajski]

Exclusive-OR (XOR) Function


- **XOR** $x \oplus y = xy' + x'y$
- **XNOR** $(x \oplus y)' = xy + x'y'$
- **Identity properties**
 - $x \oplus 0 = x; x \oplus 1 = x'$
 - $x \oplus x = 0; x \oplus x' = 1$
 - $x \oplus y' = (x \oplus y)'; x' \oplus y = (x \oplus y)'$
- **Commutative and associative**
 - $A \oplus B = B \oplus A$
 - $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$

XOR Implementation

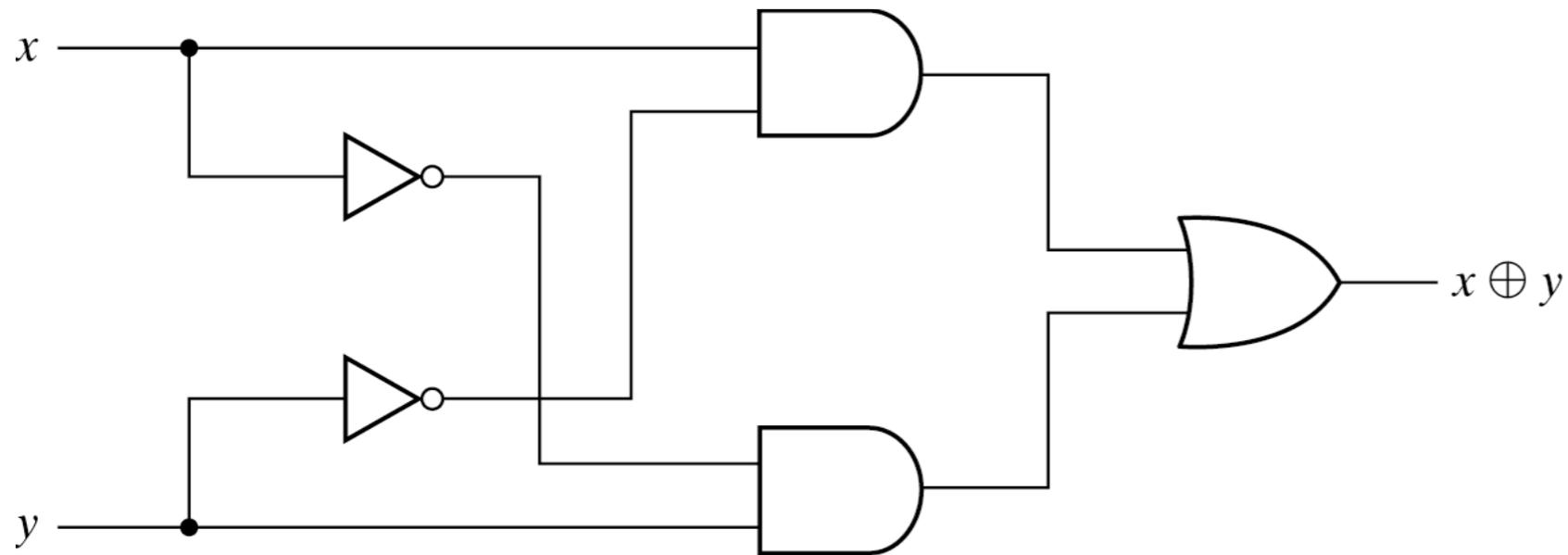- $$(x' + y')x + (x' + y')y = xy' + x'y = x \oplus y$$




(a) With AND-OR-NOT gates

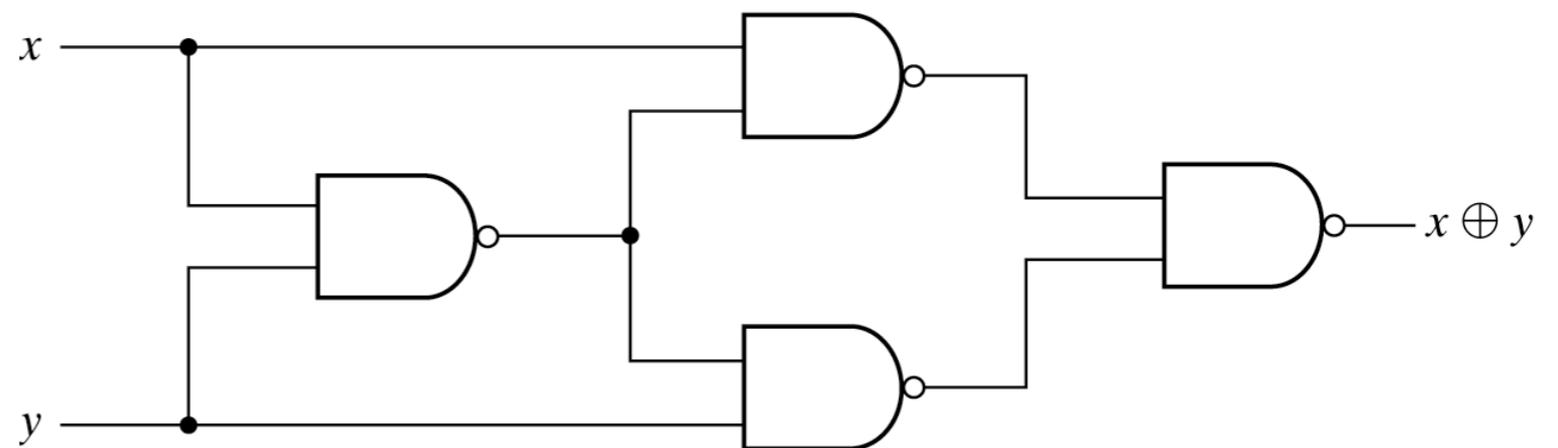

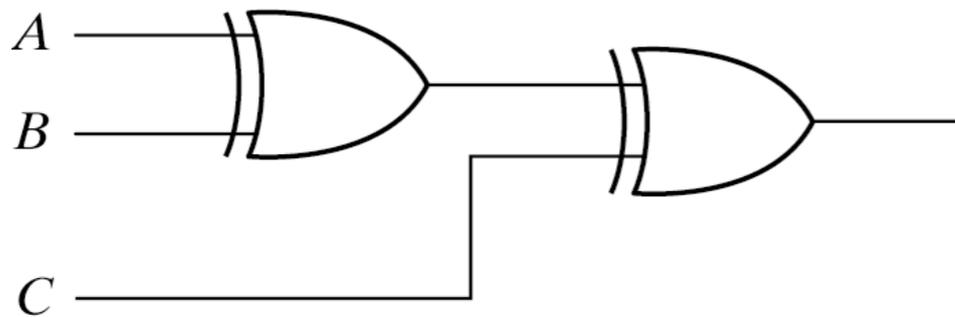
(b) With NAND gates

Odd and Even Function

$$\begin{aligned}
 A \oplus B \oplus C &= (AB' + A'B)C' + (AB + A'B')C \\
 &= AB'C' + A'BC' + ABC + A'B'C \\
 &= \sum(1, 2, 4, 7)
 \end{aligned}$$



(a) 3-input odd function

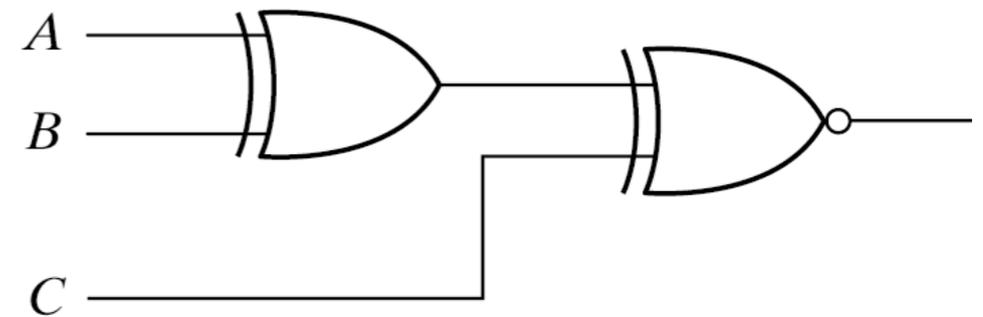

(b) 3-input even function

Parity Generation and Checking

- Parity generation


- $P = x \oplus y \oplus z$

- Parity check


- $C = x \oplus y \oplus z \oplus P$

- $C=1$: an odd number of data bit error

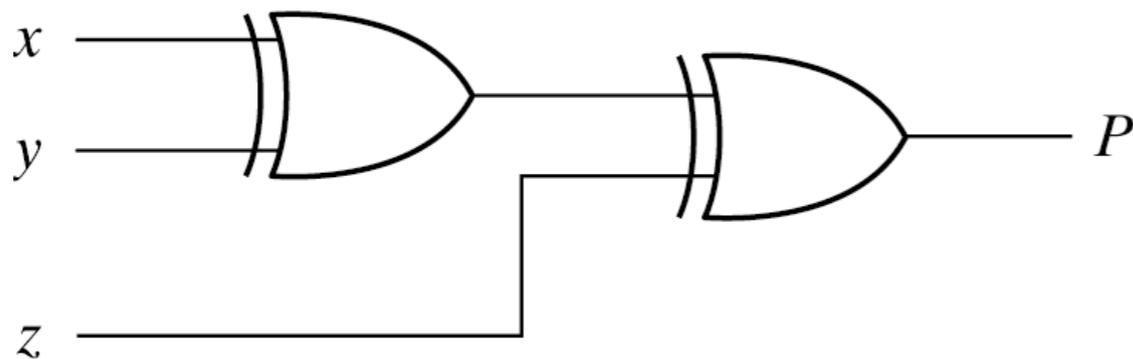- $C=0$: correct or and even # of data bit error



(a) 3-bit even parity generator

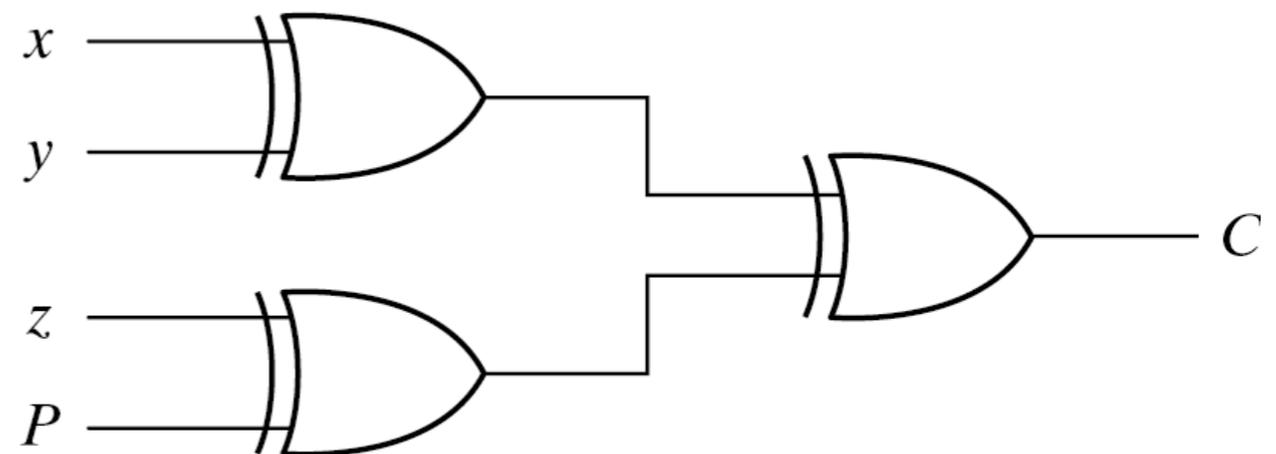

(a) 4-bit even parity checker



High-Impedance Outputs

- Three-state buffer

- Three state: 1, 0, Hi-Z
- Output: Hi-Z, Z, z (behaves as an open circuit, floating)

- Two useful properties

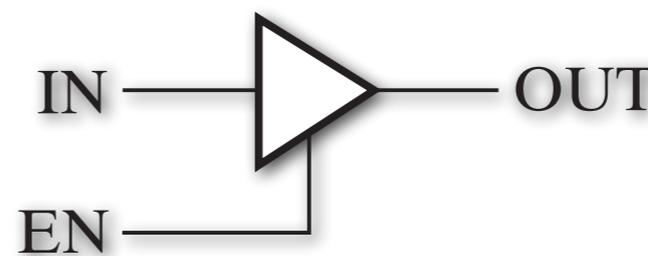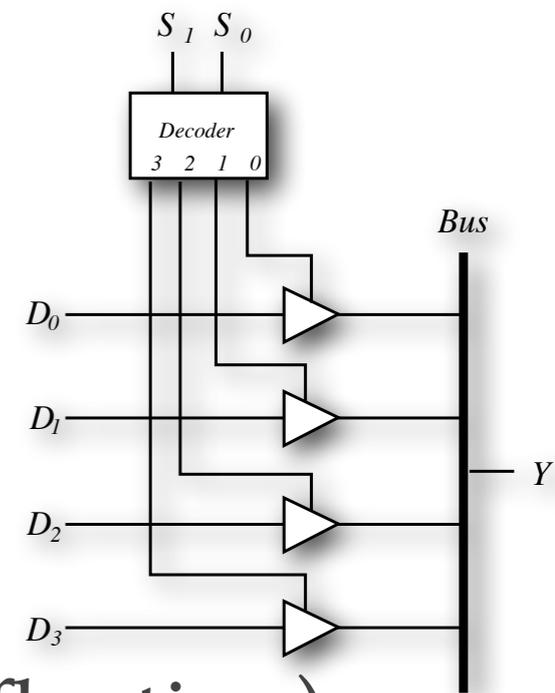- Hi-Z outputs can be connected together if no two or more gates drive the line at the same time to opposite 1 and 0 values.
- Bidirectional input/output



(a) Logic symbol

EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1

(b) Truth table